

Name: Sujam Biswas

Roll No: 302010501003

Course: BCSE (Lateral)

Group: A1

(Q) Design a counter which counts from 0 to 59.

The job of a counter is to count by advancing the contents of the counter by one count with each clock pulse. Counters which advance their sequence of numbers or states when activated by a clock input are said to operate in a "count up" mode. Likewise counters which decrease their sequence of numbers or states when activated by a clock input are said to operate in a "count down" mode. Counters can be operated in the both UP and down mode. For mode 60 counter, we design it by using a mode 10 counter that counts 0 to 9 and a mode 6 counter that counts 0 to 5.

In designing of mode 60 counter, at low means 0 it represent low counting and at high means 1, it represent high counting. At high counting, it going 0 to 59 and at low counting, it going from 59 to 0. We design the counter by using JK flip flops. We also use the clock for updown counting of the clock pulse. A clear button is used for reset the counter. To represent the count, we use LED display for counting the pulse.

JK Flip Flop Transition Table

Q_N	Q_{N+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

Designing mod 6 updown counter: \rightarrow

mode	Initial state			Final state		
	a_2	a_1	a_0	\bar{a}_2	\bar{a}_1	\bar{a}_0
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	1
0	0	1	1	0	0	0
0	1	0	0	1	0	1
0	1	0	1	1	0	0
1	0	0	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	1
1	0	1	1	0	0	0
1	1	0	0	1	0	1
1	1	0	1	1	0	0

Kmap \rightarrow

J_0	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
\bar{a}_0	1	1	X	1
a_0	X	X	X	X

$$J_0 = 1$$

J_1	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
\bar{a}_0	0	X	X	1
a_0	0	X	X	0

$$J_1 = a_2 \bar{a}_0$$

J_2	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
\bar{a}_0	1	0	X	X
a_0	0	0	X	X

$$J_2 = \bar{a}_1 \bar{a}_0$$

K_0	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
\bar{a}_0	X	X	X	X
a_0	1	1	X	1

$$K_0 = 1$$

K_1	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
\bar{a}_0	X	1	X	X
a_0	X	0	X	X

$$K_1 = \bar{a}_0$$

K_2	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
\bar{a}_0	X	X	X	1
a_0	X	X	X	0

$$K_2 = \bar{a}_0$$

Design a Up and Down (as selected by a control line)
Decade Counter using JK-Flip Flop.

S	Initial state				Final state				Input Given			
	Q_4	Q_3	Q_2	Q_1	Q_4	Q_3	Q_2	Q_1	q_1	q_2	q_3	q_4
0	0	0	0	0	0	0	0	1	1	0	0	0
0	0	0	0	1	0	0	1	0	1	1	0	0
0	0	0	1	0	0	0	1	1	1	0	0	0
0	0	0	1	1	0	1	0	0	1	1	1	0
0	0	0	0	0	0	1	0	1	1	0	0	0
0	0	1	0	1	0	1	1	0	1	1	0	0
0	0	1	1	0	0	1	1	1	1	0	0	0
0	0	1	1	1	1	0	0	0	1	1	1	1
0	1	0	0	0	1	0	0	1	1	0	0	0
0	1	0	0	1	0	0	0	0	1	0	0	1
1	0	0	0	0	1	0	0	1	1	0	0	1
1	0	0	0	1	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	0	1	1	1	0	0
1	0	1	0	0	0	0	1	1	1	1	0	0
1	0	1	0	1	0	1	0	0	1	0	0	0
1	0	1	1	0	0	1	0	1	1	1	0	0
1	0	1	1	1	0	1	1	0	1	0	0	1
1	1	0	0	0	0	1	1	1	1	1	1	1
1	1	0	0	1	1	0	0	0	1	0	0	0

For $S=0$;

Kmap S

q_2	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
$\bar{a}_4 \bar{a}_3$	0	1	1	0
$\bar{a}_4 a_3$	0	1	1	0
$a_4 \bar{a}_3$	d	d	d	d
$a_4 a_3$	0	0	d	d

$$JK \text{ for } q_2 = a_1 \bar{a}_4$$

For $S=1$,

q_2	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
$\bar{a}_4 \bar{a}_3$	0	0	0	1
$\bar{a}_4 a_3$	1	0	0	1
$a_4 \bar{a}_3$	d	d	d	d
$a_4 a_3$	1	0	d	d

$$JK \text{ for } q_2 = \bar{a}_1 a_2 + \bar{a}_1 a_3 + \bar{a}_1 a_4$$

For $S=0$

q_3	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
$\bar{a}_4 \bar{a}_3$	0	0	1	0
$\bar{a}_4 a_3$	0	0	1	0
$a_4 a_3$	d	d	d	d
$a_4 \bar{a}_3$	0	0	d	d

JK for $q_3 = a_1 a_2$

q_4	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
$\bar{a}_4 \bar{a}_3$	0	0	0	0
$\bar{a}_4 a_3$	0	0	1	0
$a_4 a_3$	d	d	d	d
$a_4 \bar{a}_3$	0	1	d	d

JK for $q_4 = a_1 a_2 a_3 + a_1 \bar{a}_4$


For $S=1$

q_3	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
$\bar{a}_4 \bar{a}_3$	0	0	0	0
$\bar{a}_4 a_3$	1	0	0	0
$a_4 a_3$	d	d	d	d
$a_4 \bar{a}_3$	1	0	d	d


JK for $q_3 = \bar{a}_1 \bar{a}_2 a_3 + \bar{a}_1 \bar{a}_2 a_4$

q_4	$\bar{a}_2 \bar{a}_1$	$\bar{a}_2 a_1$	$a_2 a_1$	$a_2 \bar{a}_1$
$\bar{a}_4 \bar{a}_3$	1	0	0	0
$\bar{a}_4 a_3$	0	0	0	0
$a_4 a_3$	d	d	d	d
$a_4 \bar{a}_3$	1	0	d	d

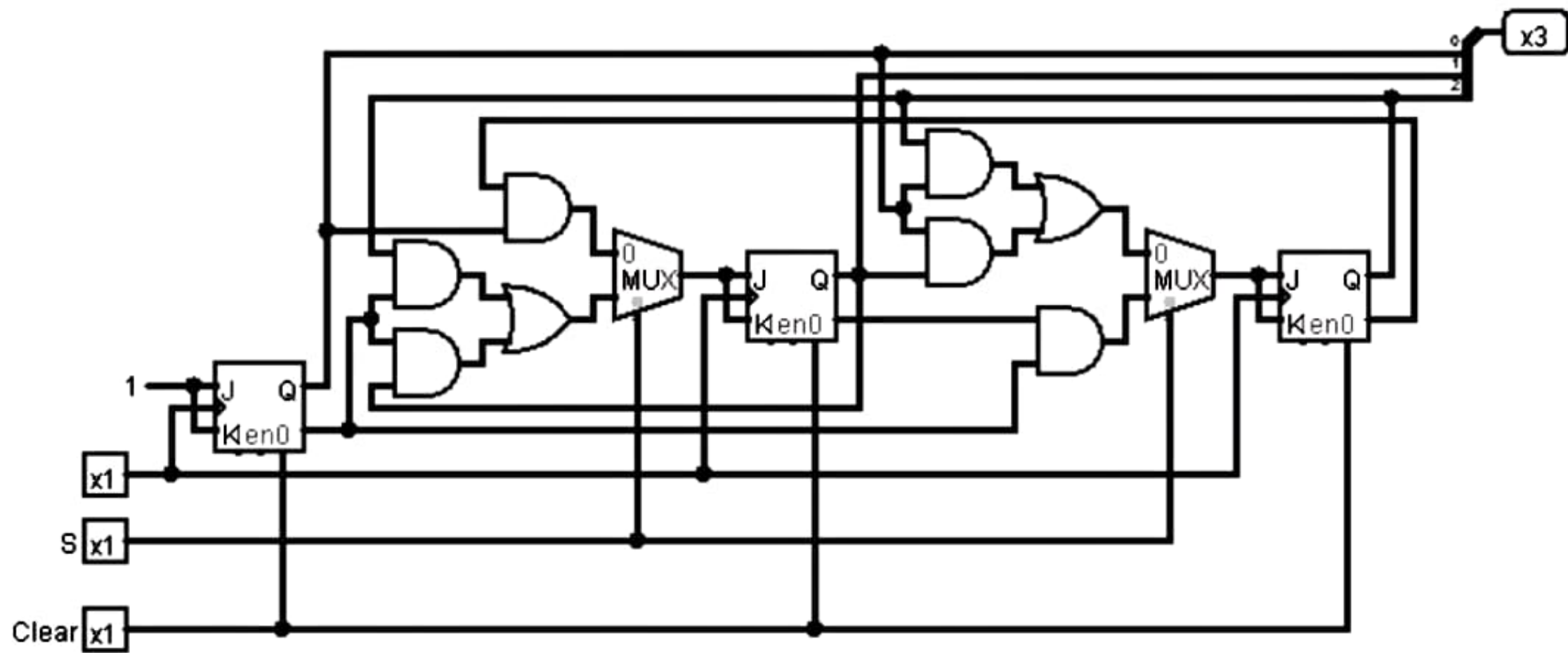
JK for $q_4 = \bar{a}_1 \bar{a}_2 \bar{a}_3$



Mod 6 counter

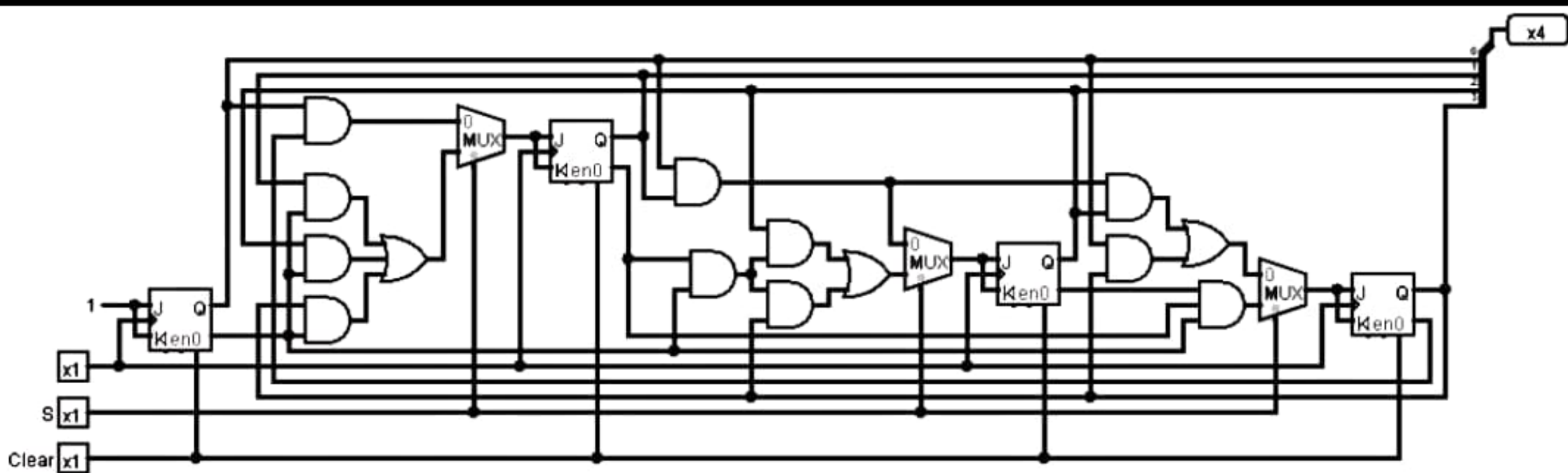

Mod 10 counter

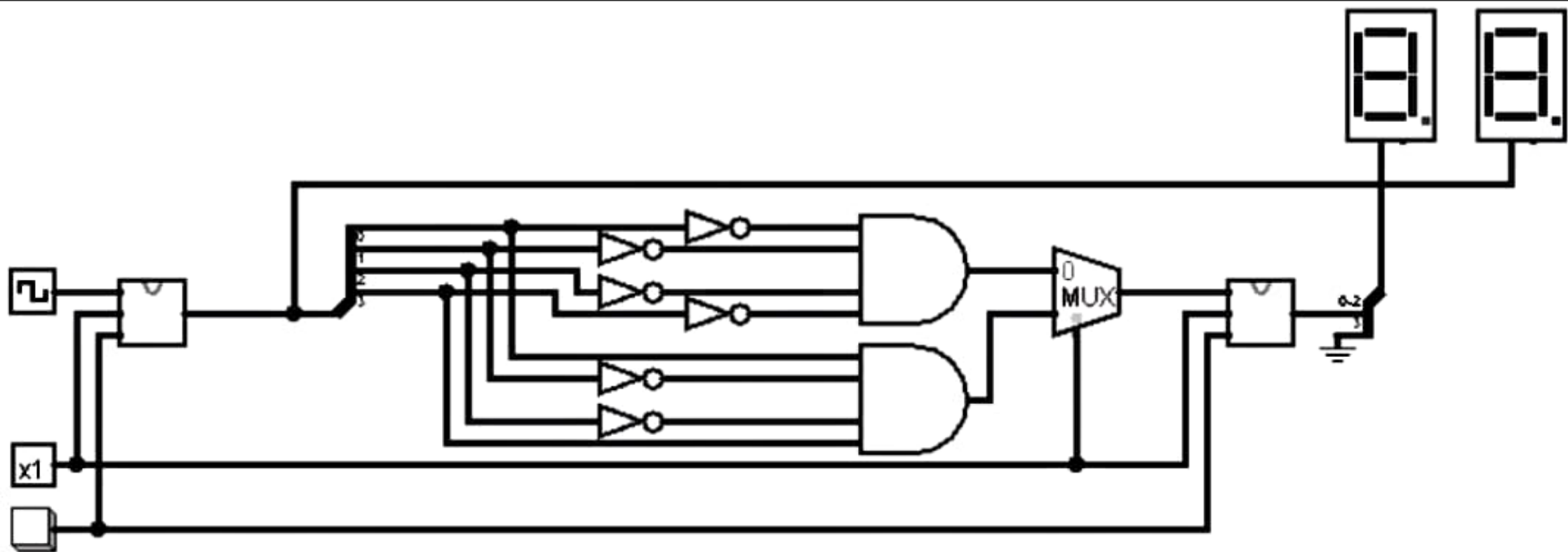

Mod 60 counter